

Electrical and Electronics Engineering Lab Report

Exp No: 03

Exp Name: *Verification of Kirchhoff's Law.*

Equipments: 1.Ammeter 2.Voltmeter 3.Bread board 4.Three resistance 5.DC power supply 6.Connecting wires

Theory:

Kirchhoff's current law(KCL) states that the algebraic sum of current entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

Kirchhoff's voltage law(KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M V_m = 0$$

Circuit diagram of KCL: The circuit diagram is look like the following figure below.

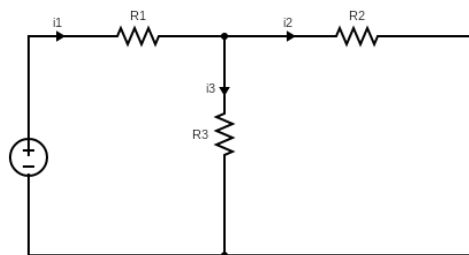


Fig 3.1: KCL Circuit diagram

Calculation:

black

Data table:

$s.n$	$voltage(V)$	I_1	I_2	I_3	$Error = \left \frac{V_s - (I_1 + I_2 + I_3)}{V_s} \right \times 100\%$
1	3	black	black	black	black%
2	4	black	black	black	black%
3	6	black	black	black	black%

Circuit diagram of KVL: The circuit diagram is look like the following figure below.

 


Fig 3.2: KVL Circuit diagram

Calculation:

black

Data table:

$s.n$	$Voltage(V_s)$	V_1	V_2	V_3	$Error = \left \frac{V_s - (V_1 + V_2 + V_3)}{V_s} \right \times 100\%$
1	3	black	black	black	black%
2	4	black	black	black	black%
3	6	black	black	black	black%

Result: blank

Discussion: blank