

# Electrical and Electronics Engineering Lab Report


**Exp No:** 05

**Exp Name:** *Verification of Thevenin's Theorem.*

**Equipments:** 1.Ammeter 2.Voltmeter 3.Bread board 4.Three resistance 5.DC power supply 6.Connecting wires

**Theory:** Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{th}$  in series with a resistor  $R_{th}$  where  $V_{th}$  is the open-circuit at the terminals and  $R_{th}$  is the input or equivalent resistance at the terminals when the independent sources are.

**Circuit diagram:** The circuit diagram looks like the following figure below.

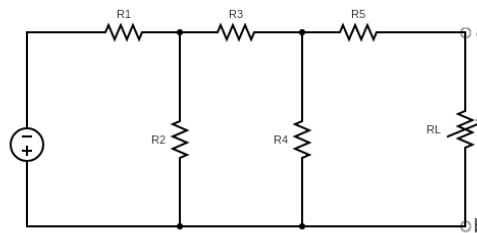

*Fig 5.1: A circuit diagram*

**Calculation:**

*Calculating  $R_{th}$ :*

$$\begin{aligned} R_{th} &= (((R_1 || R_2) + R_3) || R_4) R_5 \\ &= (((9.9 || 9.9) + 9.8) || 10) || 9.9 \\ &= 15.859 \Omega \end{aligned}$$

*Calculating  $V_{th}$ :* At loop 1:

$$\begin{aligned} -V + I_1 R_1 + R(I_1 - I_2) &= 0 \\ \Rightarrow I_1(R_1 + R_2) - I_2 R_2 &= V \\ \Rightarrow 19.8 I_1 - 9.9 I_2 &= 2 \quad \dots \quad \dots \quad \dots (1) \end{aligned}$$

At loop 2:

$$\begin{aligned} R_2(I_2 - I_1) + I_2R_3 + R_4I_2 &= 0 \\ \Rightarrow I_2(R_2 + R_3 + R_4) - I_1R_2 &= 0 \\ \Rightarrow 29.7I_2 - 9.9I_1 &= 0 \quad \dots \quad \dots \quad \dots(2) \end{aligned}$$

Now solving equation (1) and (2) we get,  $I_1 = 0.121A$ ,  $I_2 = 0.0404A$

**Data table:**

<i>s.n</i>	<i>V</i>	$V_{th}(m)$	$V_{th}(cal)$	$R_{th}(m)$	$R_{th}(cal)$	$Error_{V_{th}}$	$Error_{V_{th}}$
1	2	1.006V	1.278V	16Ω	15.859Ω	27.03%	0.889%
2	3	1.733V	1.9221V	16Ω	15.859Ω	10.91%	0.889%

**Result:** The experimental results indicates that according to Thevenin's theorem we've solved the above circuit. Though there are some problems in electronics elements of the experiment and these the cause of error.

**Discussion:** Thevenin's theorem is very esesntial law for electrical circuit for solving complex circuit diagram. From this experiment we have verified the law if there work accuracy was better. Though there are a little error, we've verified this law though there are a little error.